

**P.G. 1st Semester-2017**

**PHYSICS**

**(Electronic & Instrumentation)**

**Paper : MPHYCCT-104**

Full Marks : 50

Time : 2 Hours

*The figures in the right-hand margin indicate marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

Answer **Q. No. 1** and any **three** from the rest.

1. Answer any **five** questions:  $2 \times 5 = 10$
- a) Define frequency modulation index.
  - b) Write down the condition for maximum phase deviation in phase modulation.
  - c) Simplify the equation  
$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$
  - d) Design a first order active high pass filter having cut-off frequency of 200 Hz and a high frequency gain of 5.

- e) Write the advantages of an active filter over a passive filter. What do you mean by the bandwidth of a band pass filter.
  - f) Draw a circuit diagram of a OP-AMP based phase-shift oscillator.
  - g) Draw the band diagram of Tunnel diode at small forward biased condition.
  - h) What is direct and indirect band gap semiconductors?
2. a) Describe the working principle of a Wien-bridge oscillator with proper circuit diagram. Find an expression for the frequency of oscillator.
- b) Discuss the amplitude stability of the Wien-bridge oscillator.  $6+4=10$
3. a) Design a logarithmic amplifier with OP-AMP and describe it with proper circuit diagram.
- b) What will happen if the diode and the resistor are interchanged in logarithmic amplifier?
- c) What is D/A converter.  $5+4+1=10$
4. a) Write down the linear envelope detection process for AM wave. Derive the power relation in between the carrier wave and amplitude modulated wave.

- b) Write down the advantages of S.S.B. modulation.  $8+2=10$
5. a) Design a 1:4 De-multiplexer tree and write the expression of output.
- b) Describe the vestigial side band modulation technique.
- c) Why VSB modulation is more efficient than S.S.B. modulation?  $5+3+2=10$
6. a) Show that the product of electron and hole concentration in a semiconductor is a constant at a given temperature.
- b) Derive an expression for the width of depletion region across p-n junction in terms of impurity concentrations.  $5+5=10$
-