

2016**BCA****[HONOURS]****(Digital Logic & Computer Organization)****Paper : BCA-103**

Full Marks : 80

Time : 4 Hours

*The figures in the right-hand margin indicate marks.**Candidates are required to give their answers in their own words as far as practicable.*Answer **Question No. 1** and any **four** from the rest.

1. Answer any **eight** questions: $2 \times 8 = 16$
- Convert binary number $(101101.1101)_2$ to octal.
 - Design NOR gate using NAND gates only.
 - How many flip/flops are needed to design a mod 10 counter?
 - Write the differences between static and dynamic RAM.
 - What is race problem?
 - Find the gray code of $(101101)_2$.

[Turn over]

- Differentiate between 1's complement and 2's complement representation.
- What is CCD memory?
- What is the use of Don't Care Condition?
- Write down the truth table of S-R Flip/Flop.
- What is a ripple counter?
- What is addressing mode?

2. a) Express the following function in sum of min terms and a product of max terms
 $F(x, y, z) = (xy + z)(y + xz)$.
- b) Perform the subtraction with the following binary no's using 2's complement arithmetic:
 $(11010)_2 - (10000)_2 = ?$
- c) The sum of two no's written as 13 and 22 is 101. What is the base of the number system?
- d) Show that dual of EX-NOR is equal to its complement.
- e) Find the 10's complement of $(539)_{11}$.
 $5+3+3+3+2=16$
3. a) Simplify the following function using K-map.
 $F(A, B, C, D) = \sum(2, 3, 12, 13, 14, 15) + d(0, 4, 9)$.
- b) Design a full subtractor circuit.

- c) Implement the following function using NAND gates. Assume that both normal and complements input are available

$$F = (AB + A'B')(CD' + C'D)$$

- d) Write down the differences between BCD code and EX-3 code. $5+5+4+2=16$

4. a) Implement a Full adder circuit with multiplexer.
b) Design a combinational circuit to generate Even parity of four bit lengths.
c) Design a binary comparator to compare two binary numbers A & B each consisting of two bits. $5+7+4=16$
5. a) Explain the operation of a S-R flip/flop. What are its limitation?
b) Design a counter with the following binary sequence : 0, 4, 2, 1, 6 and repeat. Use J-K flip/flop.
c) Explain the operation of universal shift register. $4+7+5=16$
6. a) Explain the Von-Neuman architecture.
b) Discuss various data transfer techniques with the help of block diagram and timing diagram.

- c) Explain the DMA transfer process briefly. $4+8+4=16$

7. Write short notes (any **four**) : $4 \times 4 = 16$
- a) Strobe based and handshare based communication
b) Virtual Memory
c) Sequential Machine design
d) Microprogrammed control unit
e) Instruction Pipelining
f) PLAs
g) BUS